Kits and Parts dot Com

Supplying Toroids, Electronic Parts and Kits to Engineers, Schools and Hobbyists

- Home
- Create Quote
- Place Order
- Customer Portal
- Trimmer Capacitors
- NPO Disc Capacitors
- Polystyrene Capacitors
- Silvered Mica Capacitors
- Crystals - Matched
- W3NQN Filters
- WA2EBY Toroid Kit
- Variable Inductors
- Magnet Wire
- Diodes
- Integrated Circuits
- Jacks Plugs
- Transistors - Fets
- Misc Parts
- RFtoolkits
- Organic 5Watter Kits
  Transceivers for 17,20,30,40 Meters
- Toroids
- Retired Kits
- SMT Parts
- Contact
- FAQ

Build this Universal SWR bridge V1.5
Note that there are many FAKE versions on Ebay.

PDF Instructions in Spanish submitted of Jon, EA2SN

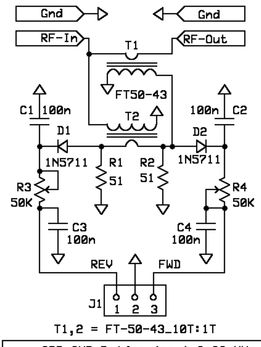

T1,2 = FT-50-43_10T:1T

QRP SWR Bridge for 1.8-30 MHz		
Kits And Parts Dot Com		
by WB0IZ	Rev 1.4	29 Oct 2018

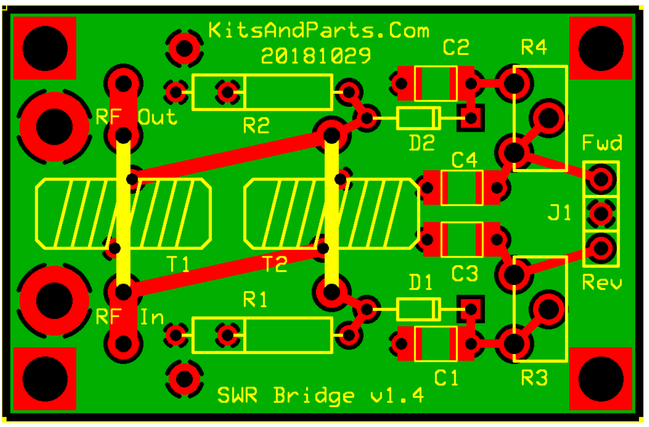

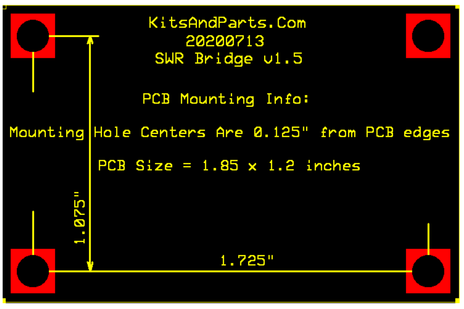

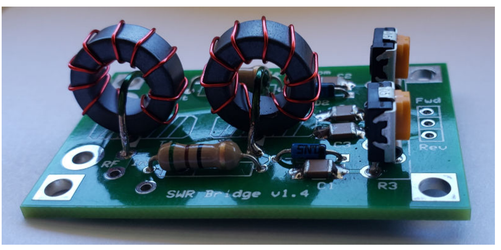

Building Instructions:

1. Inventory all Parts

2. Install all Resistors.

____R1,2: 51 (1/2 Watt) Green-Brown-Black-Gold
Note: R3,4 controls the output of the SWR bridge.
____R3,4: 50K ohm pot

3. Install all capacitors.

____C1,2,3,4: SMT or 100n brown labeled 104 or green 104
We highly recommend installing the SMT caps vs the thru hole types
The SMT caps provide better RF shunting to ground

4. Install the detector Diodes.
____D1,2: 1N5711 - install flush against PCB per parts markings
Do not overheat when soldering.

5. Wind and install the RF coupling transformers.

____T1 & T2: Wind 10/12 turns of 26 ga red or green wire on both FT50-43 ferrite toroids.
For 3.5 - 30 MHz, use 10 turns (more sensitive at low power)
For 1.8 - 30 MHz, use 12 turns (less sensitive at low power)
Cut the 20 inches of red magnet wire in half.
Wind the wires (10" each) on the toroids clockwise.
Trim the wires of T1 & T2 to a half inch.
Strip the insulation off the wires using a very hot solder pencil and solder.
Install the wound toroids on the PCB and trim leads from the PCB.

Cut the 2 inches of #20 green magnet wire in half.
Earlier versions of the SWR kit use surplus resistor leads.
Strip the insulation off of 0.25 inches (6.3 mm) on all 4 ends of the wires
Bend the wires in a "U" shape using a standard size pencil.
Install the leads thru T1 & T2 with the wire going thru the center of the toroid
Solder the leads on the bottom of the PCB.

6. Connections.
Connect the bridge to a 5W RF source(in) and a 50 ohm dummy load(out).
Connect two mechanical meters to J1 or one meter with a SPDT switch.
Suggest using 50 uA, up to 2 mA mechanical meters.
Note: Meters are NOT supplied in the kit.
Adjust both R3 & R4 to mid-range.
Apply 5 Watts and adjust R4 for a full scale reading.
Reverse the RF connections so that the dummy load is at the input.
Apply 5 Watts and adjust R3 for a full scale reading.
The SWR Meter is now ready to use (5 watts full scale).
Designed for a maximum of 100 Watts (intermittent).